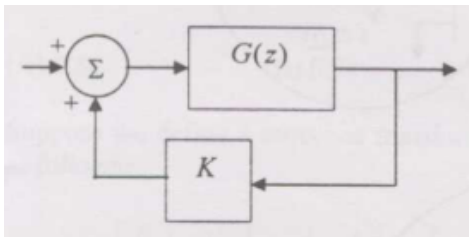


## 2007-EE

ee24btech11064 - Harshil Rathan

- 1) The system  $\frac{900}{s(s+1)(s+9)}$  is to be compensated such that its gain-crossover frequency becomes the same as its uncompensated phase-crossover frequency and provides a  $45^\circ$  phase margin. To achieve this, one may use:
  - a) a lag compensator that provides an attenuation of  $20dB$  and a phase lag of  $45^\circ$  at the frequency of  $3\sqrt{3}$  rad/s
  - b) a lag compensator that provides an amplification of  $20dB$  and a phase lead of  $45^\circ$  at the frequency of  $3$  rad/s
  - c) a lag-lead compensator that provides an amplification of  $20dB$  and a phase lag of  $45^\circ$  at the frequency of  $\sqrt{3}$  rad/s
  - d) a lag-lead compensator that provides an attenuation of  $20dB$  and a phase lead of  $45^\circ$  at the frequency of  $3$  rad/s
- 2) Consider the discrete-time system shown in figure where the impulse response of  $G(z)$  is  $g(0) = 0, g(1) = g(2) = 1, g(3) = g(4) = \dots = 0$  This system is stable for range of values


of  $K$ 

- a)  $[-1, \frac{1}{2}]$                       c)  $[\frac{-1}{2}, 1]$   
b)  $[-1, 1]$                          d)  $[\frac{-1}{2}, 2]$
- 3) A signal  $x(t)$  is given by


$$x(t) = \begin{cases} 1, & -\frac{T}{4} < t \leq \frac{3T}{4} \\ -1, & \frac{3T}{4} < t \leq \frac{7T}{4} \\ -x(t+T) & \text{(periodic extension)} \end{cases}$$

Which among the following gives the fundamental Fourier term of  $x(t)$ ?

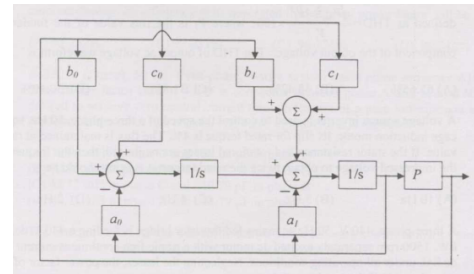- a)  $\frac{4}{\pi} \cos(\frac{\pi T}{T} - \frac{\pi}{4})$                       c)  $\frac{4}{\pi} \sin(\frac{\pi T}{T} - \frac{\pi}{4})$   
b)  $\frac{\pi}{4} \cos(\frac{\pi T}{2T} - \frac{\pi}{4})$                       d)  $\frac{\pi}{4} \sin(\frac{\pi T}{2T} - \frac{\pi}{4})$
- 4) If the loop gain K of a negative feedback system having a loop transfer function  $\frac{K(s+3)}{(s+8)^2}$  is to be adjusted to induce a sustained oscillation then
- a) The frequency of this oscillation must be  $\frac{4}{\sqrt{3}}$  rad/s  
b) The frequency of this oscillation must be 4 rad/s  
c) The frequency of this oscillation must be 4 or  $\frac{4}{\sqrt{3}}$  rad/s  
d) such a K does not exist
- 5) The system shown in figure below can be




reduced to the form

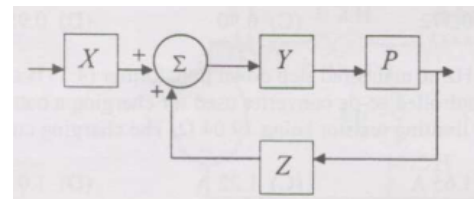

- a)  $X = c_0s + c_1$ ,  $Y = \frac{1}{s^2 + a_0s + a_1}$ ,  $Z = b_0s + b_1$
  - b)  $X = 1$ ,  $Y = \frac{c_0s + c_1}{s^2 + a_0s + a_1}$ ,  $Z = b_0s + b_1$
  - c)  $X = c_1s + c_0$ ,  $Y = \frac{b_1s + b_0}{s^2 + a_1s + a_0}$ ,  $Z = 1$
  - d)  $X = c_1s + c_0$ ,  $Y = \frac{1}{s^2 + a_1s + a_0}$ ,  $Z = b_1s + b_0$
- 6) The value of  $\oint_C \frac{dz}{(1+z^2)}$  where C is contour  $|z - \frac{i}{2}| = 1$  is

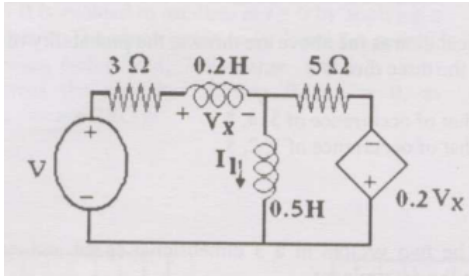- a)  $2\pi i$                       c)  $\tan^{-1} z$   
 b)  $\pi$                           d)  $\pi i \tan^{-1} z$
- 7) A single-phase voltage source inverter is controlled in a single pulse-width modulated mode with a pulse width of  $150^\circ$  in each half cycle. Total harmonic distortion is defined as  $THD = \frac{\sqrt{V_{rms}^2 - V_1^2}}{V_1} \times 100$ , where  $V_1$  is the rms value of the fundamental component of the output voltage. The THD of output ac voltage waveform is
- a) 65.65%                      c) 31.83%  
 b) 48.42%                      d) 30.49%
- 8) A voltage source inverter is used to control the speed of a three-phase, 50Hz, squirrel cage induction motor. Its slip for rated torque is 4%. The flux is maintained at rated value. If the stator resistance and rotational losses are neglected, then the frequency of the impressed voltage to obtain twice the rated torque at starting should be
- a) 10Hz                          c) 4Hz  
 b) 5Hz                          d) 2Hz
- 9) A three-phase, 440V, 50Hz ac mains fed thyristor bridge is feeding a 440Vdc, 15kW, 1500rpm separately excited dc motor with a ripple free continuous current in the dc link under all operating conditions. Neglecting the losses, the power factor of the ac mains at half the rated speed, is
- a) 0.354                          c) 0.90  
 b) 0.372                          d) 0.955
- 10) A single-phase, 230V, 50Hz ac mains fed step down transformer (4 : 1) is supplying power to a half-wave uncontrolled ac-dc converter used for charging a battery (12Vdc) with the series current limiting resistor being  $19.04\Omega$ . The charging current is
- a) 2.43A                          c) 1.22A  
 b) 1.65A                          d) 1.0A
- 11) A three-phase synchronous motor connected to ac mains is running at full load and unity power factor. If its shaft load is reduced by half, with field current held constant, its new power factor will be
- a) unity  
 b) leading  
 c) lagging  
 d) dependent on machine parameters
- 12) A 100kVA, 415V (line), star-connected synchronous machine generates rated open circuit voltage of 415V at a field current of 15A. The short circuit armature current at a field current of 10A is equal to the rated armature current. The per unit saturated synchronous reactance is
- a) 1.731                          c) 0.666  
 b) 1.5                              d) 0.577
- 13) A three-phase, three-stack, variable reluctance step motor has 20 poles on each rotor and stator stack. The step angle of this step motor is
- a)  $3^\circ$                               c)  $9^\circ$   
 b)  $6^\circ$                               d)  $18^\circ$
- 14) A single-phase 50kVA, 250V/500V two winding transformer has an efficiency of 95% at full load, unity power factor. If it is reconfigured as 500V/750V autotransformer, its efficiency at its new rated load at unity power factor will be
- a) 95.752%                      c) 98.276%  
 b) 97.851%                      d) 99.241%
- 15) A 230V(Phase), 50Hz, three-phase, 4-wire system has a phase sequence ABC. A unity power-factor load of 4kW is connected between phase A and neutral N. It is desired to achieve zero neutral current through the use of a pure inductor and a pure capacitor in the other two phases. The value of inductor and capacitor is
- a) 72.95mH in phase C and  $139.02\mu F$  in phase B  
 b) 72.95mH in phase B and  $139.02\mu F$  in phase C  
 c) 42.12mH in phase C and  $240.79\mu F$  in phase B  
 d) 42.12mH in phase B and  $240.79\mu F$  in phase C
- 16) The state equation for the current  $I_1$  shown in the network shown below in terms of the

voltage  $V_x$  and the independent source  $V$ , is given by



- a)  $\frac{dI_i}{dt} = -1.4V_x - 3.75I_i + \frac{5}{4}V$   
 b)  $\frac{dI_j}{dt} = 1.4V_3 - 3.75I_j - \frac{5}{4}V$   
 c)  $\frac{dI_i}{dt} = -1.4V_s + 3.75I_i + \frac{5}{4}V$   
 d)  $\frac{dI_j}{dt} = -1.4V_x + 3.75I_t - \frac{5}{4}V$
- 17) If  $u(t)$ ,  $r(t)$  denote the unit step and unit ramp functions respectively and  $u(t)*r(t)$  their convolution, then the function  $u(t+1)*r(t-2)$  is given by
- a)  $\left(\frac{1}{2}\right)(t-1)(t-2)$       c)  $\left(\frac{1}{2}\right)(t-1)^2 u(t-1)$   
 b)  $\left(\frac{1}{2}\right)(t-1)(t-2)$       d) none of the above